CS 2461 Lab- Week 5

Today....

- Review Design of Finite State Machines example
- Bitwise operations in C complete the exercise from lecture course webpage – Exercises-Week5 download sept27.c

Finite State Machines

- The behavior of sequential circuits can be expressed using finite state machines (FSMs).
 - FSMs consist of a set of nodes that hold the states of the machine and a set of arcs that connect the states.
 - FSM represented as a graph

Elements of FSM:

- Finite Number of states
- Finite number of inputs and Finite number of outputs
- A specification of the state transitions
- A specification (Boolean function) of the outputs
- Outputs are associated with a node/state

FSM Design Process

- The first step is to model the behavior of the machine
 - Based on problem statement
 - Identify what the inputs are
 - Identify the outputs
 - Determine what needs to be stored to capture the "state" of the machine
- Represented as a graph finite state diagram
 - Nodes: States a state stores summary of events (until current time)
 - Edges: Transition from current state to next state
 - Based on input and current state and computed by combinational logic
 - Outputs: value of outputs at each state
 - State: the state of a system is a "snapshot" of all relevant elements at an instant in time.

• Example : vending machine should remember total money received,....

Designing and implementing a FSM

- 1. Understand the problem statement and determine inputs/outputs
- 2. Identify states and draw the state diagram
 - Encode each state in binary using N bits
 - State diagram will show transitions from state to state based on value of inputs
- 3. Next, derive the truth table (from state diagram)
 - "inputs" in truth table are N current state variables and the inputs
 - These N state variables will need to be stored in N flips flops,
 - Label the N state variables $S_{N-1}S_{N-2}...S_1S_0$
 - "outputs" are the values of the state variables in the next state and the output at each state -- common notation is S' but confusion with complement operator, so let's use S*
- 4. From truth table, implement combinational circuit (boolean function) for each of the next state values & outputs
 - State variables are stored in your N storage elements

FSM Design: Example

- design the finite state diagram for a sequential circuit that generates an output Z=1 whenever the input (binary) string it has read thus far has an odd number of 0's and an odd number of 1's.
 - For example, if the input string is 010010 (4 zeros and 2 ones) then output Z=0. If the input string is 1101 (1 zeros and 3 ones) then the output is Z=1.
- Assume: at each clock cycle the machine reads one bit (a 0 or 1)
 - Eg. If overall input = 0101 then after 2 cycles it would have read 01 (and output=1),

after 3 cycles it has read 010 (and output =0), etc.

Question: What property in a state ?

- The first 'property' to note is that for any binary string, the string has some X number of 1's and some Y number of 0's.
 - For string 01100 we have *X*=2 and *Y*=3
- The question is now defined in terms of the properties of X and Y
 if X and Y are both odd then output Z=1
- For any binary string how many cases can you have in terms of the evenness/oddness of X and Y?
- Four cases = Four states:
 - 1. X even and Y even
 - 2. X even and Y odd
 - 3. X odd and Y even
 - 4. X odd and Y odd

State transitions

- you have 4 cases for any binary string of any length; next, what happens if a string that has been processed (i.e., read) thus far falls under case 3 (i.e., X is odd and Y is even) and then the machine reads a 1
- String (thus far) now has X is even and Y is even = Case 1
- you have 4 cases for any binary string of any length; next, what happens if a string that has been processed (i.e., read) thus far falls under case 3 (i.e., X is odd and Y is even) and then the machine reads a 0
- = X is odd and Y is odd = Case 4

Complete the transitions

- Case1 (State1): X even and Y even
 - Read 0 go to ?
 - Read 1 go to ?
- Case 2 (State 2): X even and Y odd
 - Read 0 go to ?
 - Read 1 go to ?
- Case 3 (State 3): X odd and Y even
 - Read 0 go to ?
 - Read 1 go to ?
- Case 4 (State 4): X odd and Y odd
 - Read 0 go to ?
 - Read 1 go to ?

X = no. of 1's in string Y = no. of 0's in string

States:

- 1. X even and Y even
- 2. X even and Y odd
- 3. X odd and Y even
- 4. X odd and Y odd

Draw the finite state diagram



Truth table

- How many state variables (storage bits) ?
- 2 bits $-S_1 S_0$
 - State1 = 00 State2 = 01 State3 = 10 State4 = 11
- If FSM is in State1 (00) and input=0 then next state is 01 and current output in State00 is Z=0
- In=0 $S_1 = 0$ $S_0 = 0$ then $S_1^* = 0$ $S_0^* = 1$ Z=0
- If FSM is in State 4 (11) and input=1 then next state is 01 and current output in State11 is Z=1
- In=1 $S_1 = 1$ $S_0 = 1$ then $S_1^* = 0$ $S_0^* = 1$ Z=1

Complete the Truth Table

In	S1	S0	S1*	S0*	Z
•					•
0	0	0	U	1	U
0	0	1	0	0	0
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	0	1	1

Questions on Finite State Machines ?

Bitwise operations in C

Go to course website Download Exercises Week 5 – Sept27.c (under C and Data Rep) (do not compile and run it yet!)

C data types and operators

- Unsigned and signed int C allows casting
- Bitwise operations:
 - & (and)
 - | (or)
 - ~ (complement)
 - ^ (XOR)
 - Right shift >> arithmetic shift = MSB is replicated rightwards shift
 - Left shift << shift in 0's into the LSBs

 \circ What is left shift one position ? What is the value of (x <<1) ?

- Logical operators: arguments are treated as binary (True or false)
 - && (logical And)
 - || (logical OR)
 - ! (logical NOT)
 - Key takeaway: if x is a non-zero integer then x is True

Time to test your C ...

- Download/open Exercises-Week5 (a C file called sept27.c) from webpage
- **Do NOT run the C code**....Go through code and answer the questions without running the code
 - Reading code (without running it) is a very important skill
- Use the following values as inputs (this info included in the comments in C file):
 - zz = abcd0123 (hex representation of a 32 bit number)
 - a=4, b=7, n=2 and different values of c for c>0, c<0, and c=0
- 1. First answer the questions
- 2. Next: Compile and run your code & compare your answers with the run-time results
- 3. Can you explain what is going on (if your answer did not match)

Notation: a prefix of 0x indicates Hex representation 0x25 is the integer $2*16^1 + 5*16^0 = 37$ 0xFF is the integer with 1's in last 8 bits, i.e., decimal value 255

CallMeNext

}

```
int CallMeNext(int x){
```

```
int t;
t= (1 <<x); what is 1 << 1? What is 1 << 2?
t= t+1; what is 1 << x?
return (t);
```

CallMeLast

}

```
int CallMeLast(int x, int y){
```

```
int temp;
temp = ~y; computes complement of y (invert all bits)
temp = temp +1; what is temp= (NOT y)+1 ?
temp = temp + x;
return(temp);
```

```
■ whoaml 0 < n ≤ 3</p>
int whoamI(int x, int n){
  int rs;
   int y = n << 3; what is y when n=2? What happens when you
          shift an integer left 3 places?
   int xs = 0xFF << y; what is oxFF left shifted 16 places
   rs= xs & x; what bits (bytes) are you masking?
   /* return(rs); */
    return ((rs >> y)& 0xFF);
}
   Example: x = 0x abcd1234 and n = 2
   What is y = 2 <<3 = 2*8 = 16
   What is xs = 0xFF << 16 = 0x 00FF0000
   What is rs = 00FF0000 & abcd1234 = ?
```

WhatamI

```
int whatamI(int A) {
```

```
int X,Y;
X = (A ^ (-A)) >> 31; suppose Z= (A ^ (-A)) then what is the least
            significant bit of X in terms of Z?
Y = (X & 0x1); when is Y=1? When is Y=0?
return(Y);
```

}

```
think of the binary representation of integers A and -A
if A=12 in binary = 0000.....1010 and 0x 0000 000C in Hex
What is -A = -12 in binary ?
then what is the MSB of (A ^ (-A))
```